

# Unit 4

## Lecture 4

# Multiplexers

- A digital multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines.
- Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.

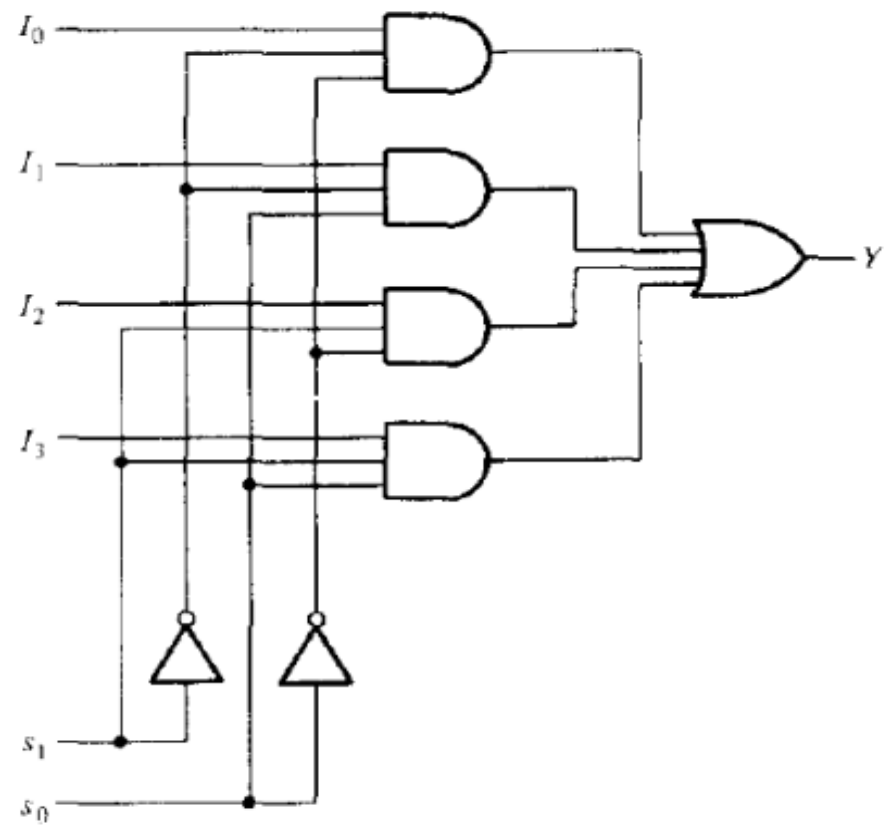


Fig: Logic Diagram: 4-to-1 line Multiplexer

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

Table: Function table

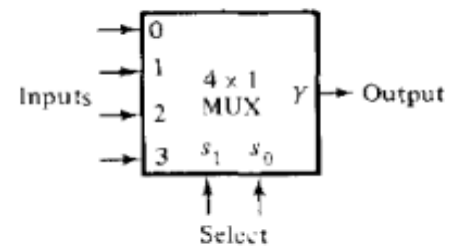



Fig: Block Diagram of Multiplexer

# Demultiplexer

- A demultiplexer is a circuit that receives information on a single line and transmits this information on one of  $2^n$  possible output lines.
- The selection of a specific output line is controlled by the bit values of  $n$  selection lines.
- A Decoder with an enable input can function as a demultiplexer.
- Here, enable input and input variables for decoder is taken as data input line and selection lines for the demultiplexer respectively.
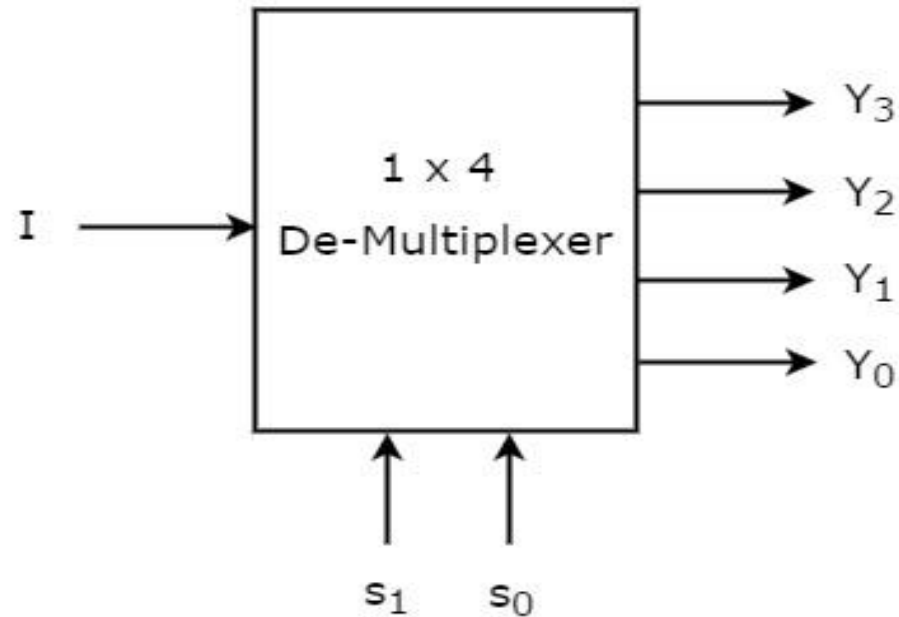
# 1x4 De-Multiplexer

*1x4 De-Multiplexer has one input  $I$ , two selection lines,  $s_1$  &  $s_0$  and four outputs  $Y_3$ ,  $Y_2$ ,  $Y_1$  &  $Y_0$ . The **block diagram** of 1x4 De-Multiplexer is shown in the following figure.*



*The single input 'I' will be connected to one of the four outputs,  $Y_3$  to  $Y_0$  based on the values of selection lines  $s_1$  &  $s_0$ . The **Truth table** of 1x4 De-Multiplexer is shown below*

Selection Inputs		Outputs			
$s_1$	$s_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

From the above Truth table, we can directly write the **Boolean functions** for each output as

$$\begin{aligned} Y_2 &= S_1 S_0' I \\ Y_1 &= S_1' S_0 I \\ Y_0 &= S_1' S_0' I \end{aligned}$$

*From the above Truth table, we can directly write the **Boolean functions** for each output as*

$$Y_3 = S_1 S_0 I$$

$$Y_2 = S_1 S_0' I$$

$$Y_1 = S_1' S_0 I$$

$$Y_0 = S_1' S_0' I$$

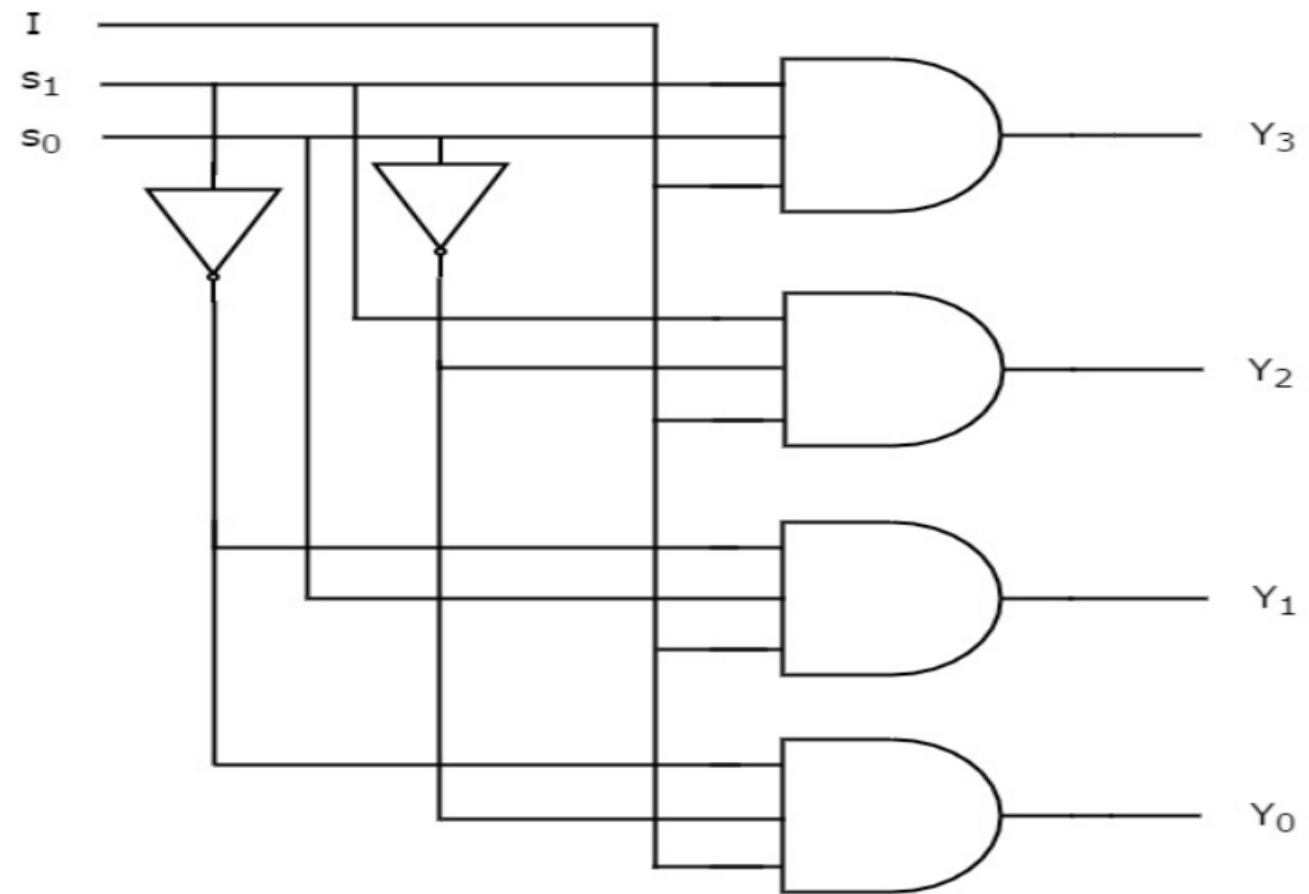


Fig: Logic Diagram